

Experiment 5 Preliminary Work

Frequency Response

Ahmet Akman 2442366

May 15, 2022

Contents

1	Step 1	1
2	Step 2	2
3	Step 3	2
3.1	a.	3
3.2	b.	3
4	Step 4	3
4.1	a.	3
4.2	b.	3
4.3	c.	3
4.4	d.	4
5	Step 5	4
6	Step 6	4
6.1	a.	4
6.2	b.	5
6.2.1	i.	5
6.2.2	ii.	6
6.3	c.	7
6.3.1	i.	7
6.3.2	ii.	8
6.3.3	iii.	8
7	Conclusion	9

1 Step 1

The document entitled "Notes on Frequency Response" is read.

2 Step 2

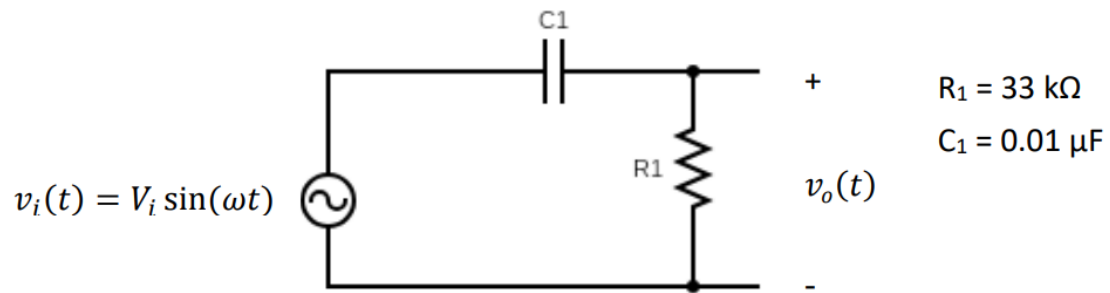


Figure 1: RC Filter circuit schematic for the step 2

3 Step 3

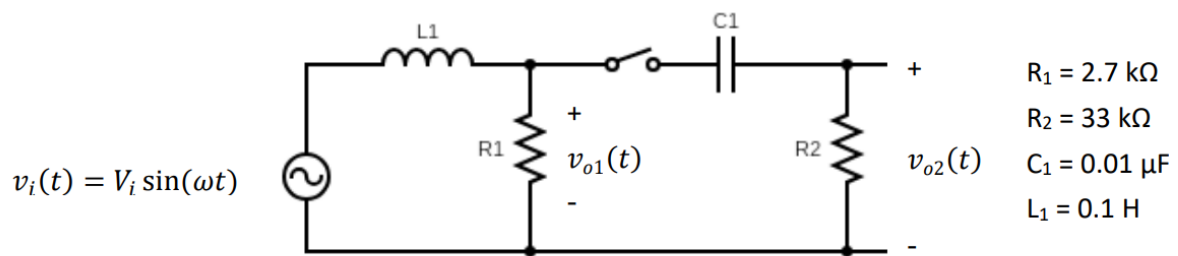


Figure 2: Low-Q RC Filter circuit schematic for the step 3

3.1 a.

3.2 b.

4 Step 4

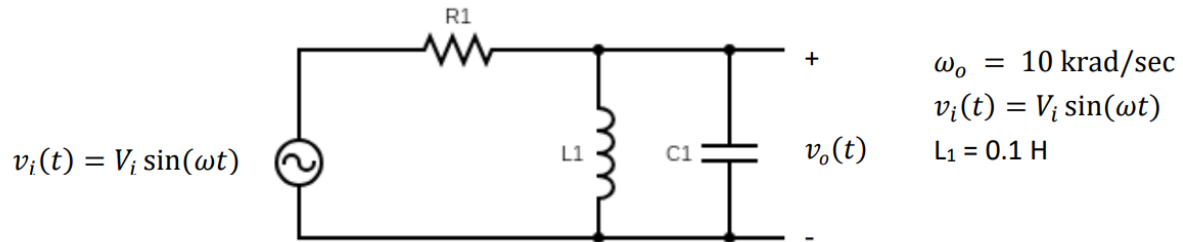


Figure 3: High-Q RC Filter circuit schematic for the step 4

4.1 a.

4.2 b.

4.3 c.

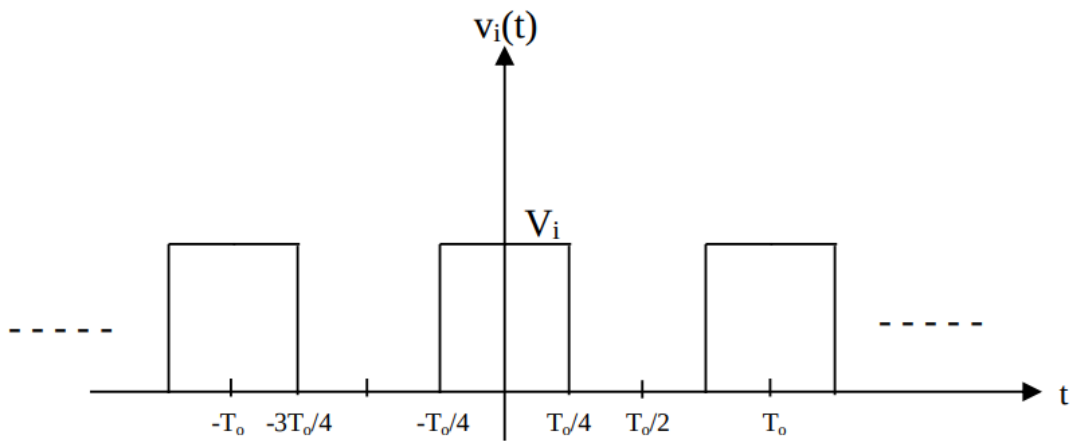


Figure 4: Input waveform

4.4 d.

5 Step 5

6 Step 6

In this step necessary simulations are made.

6.1 a.

The circuit given in Figure 1 is simulated in LTSpice simulation environment as given in Figure 5.

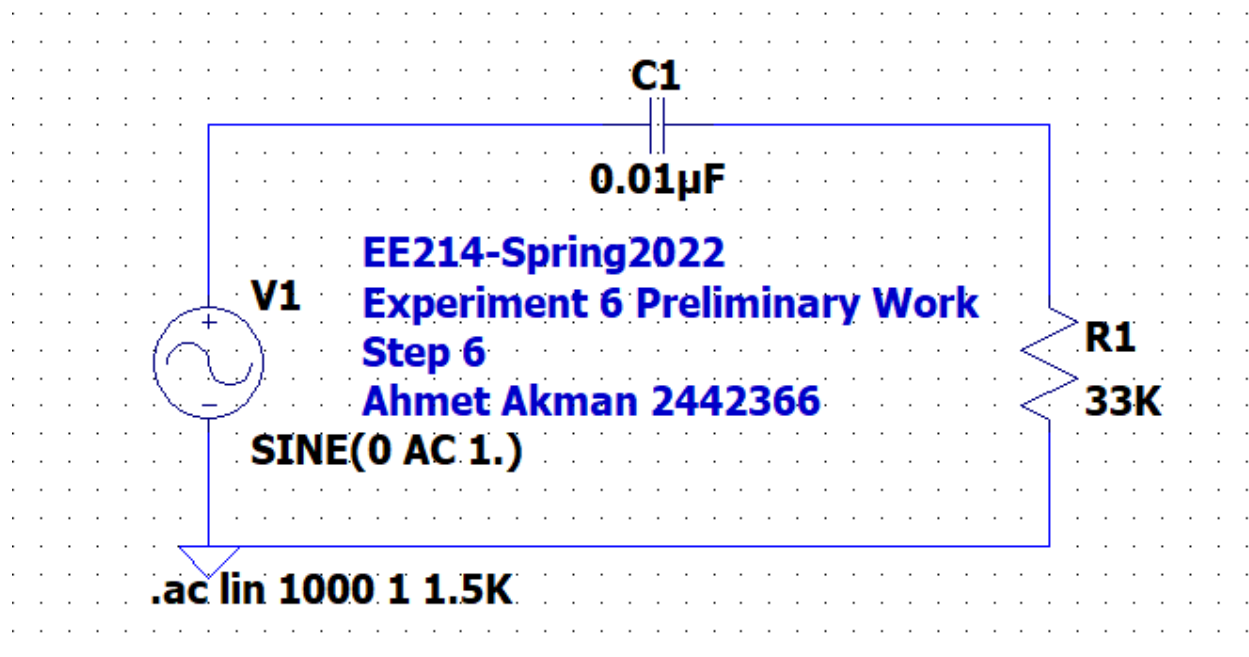


Figure 5: Simulation circuit schematic for the step 6 part a

As a result the plot given in Figure 6 is obtained.

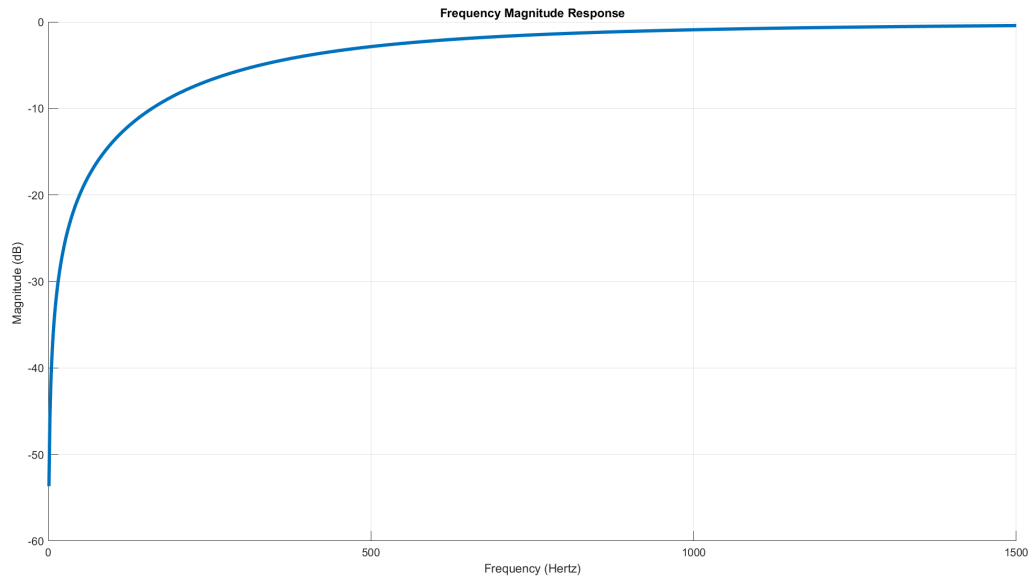


Figure 6: Frequency Response of a High Pass Filter

6.2 b.

The circuit given in Figure 2 is simulated in LTSpice simulation environment as given in Figure 7.

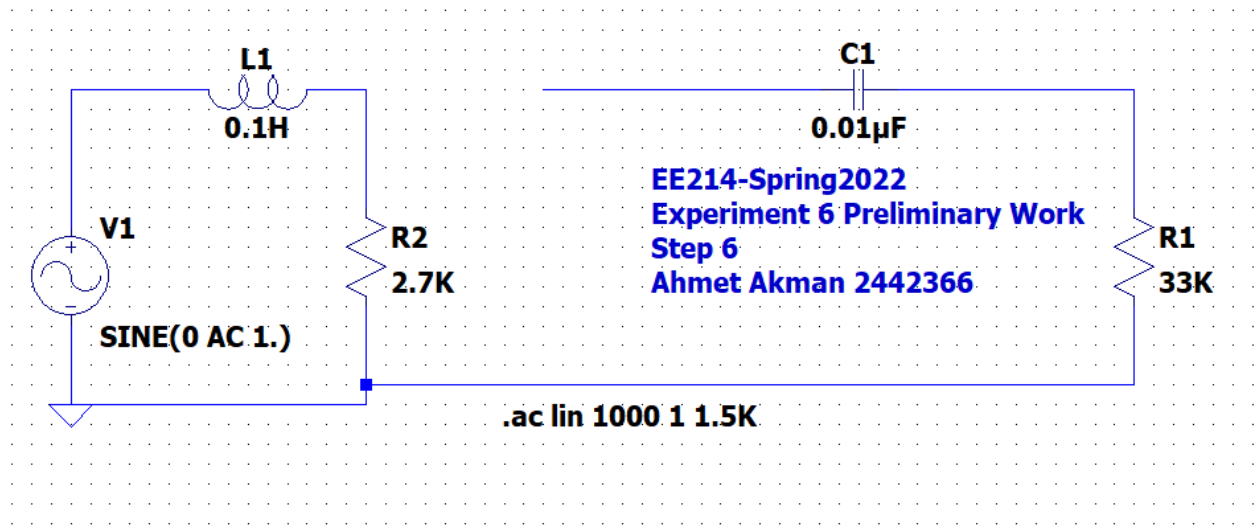


Figure 7: Simulation circuit schematic for the step 6 part b

6.2.1 i.

As the switch opened the plot given in Figure 8 is obtained.

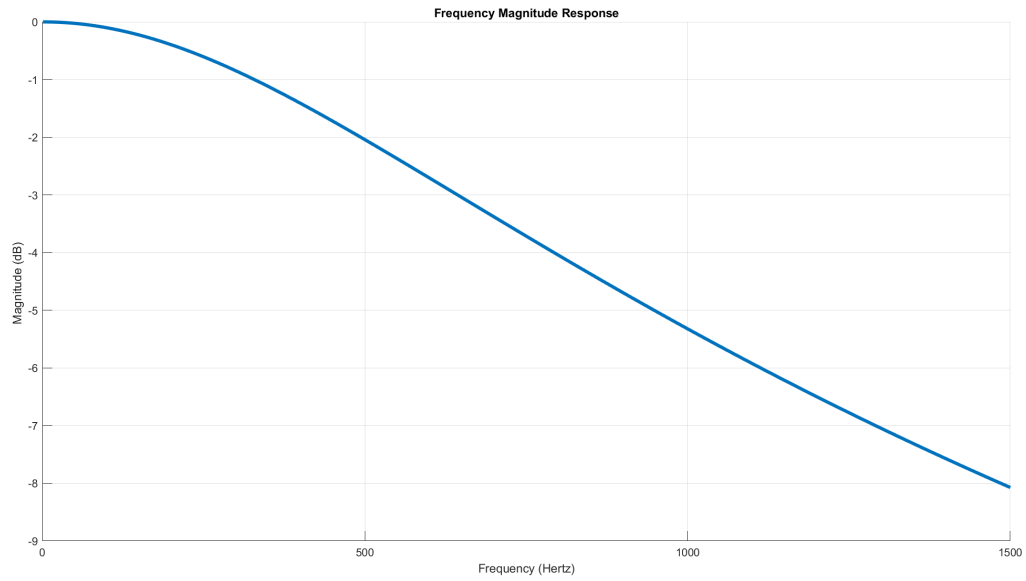


Figure 8: Frequency Response of a Low Pass Filter

6.2.2 ii.

As the switch closed the plot given in Figure 9 is obtained.

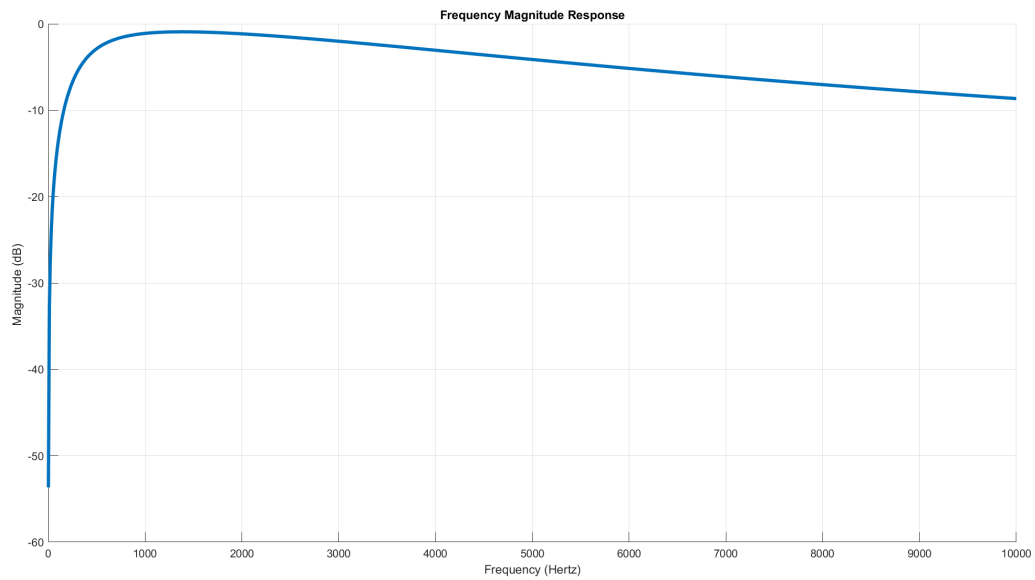


Figure 9: Frequency Response of a Band Pass Filter

6.3 c.

The circuit given in Figure 3 is simulated in LTSpice simulation environment as given in Figure 10. The capacitor value is fixed as $0.1\mu F$

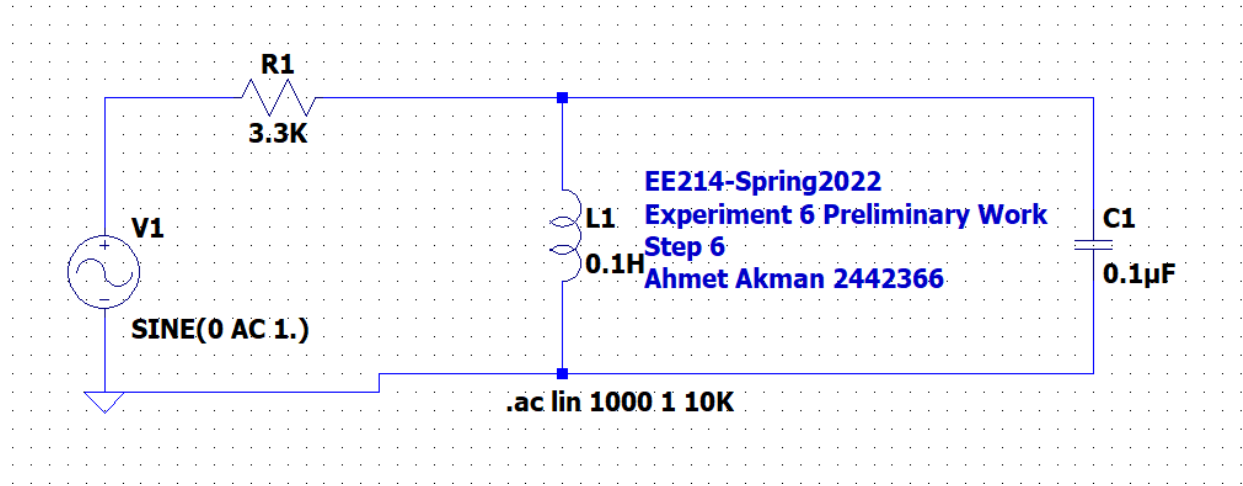


Figure 10: Simulation circuit schematic for the step 6 part c

6.3.1 i.

As the resistor value set to 3.3K the plot given in Figure 11 is obtained.

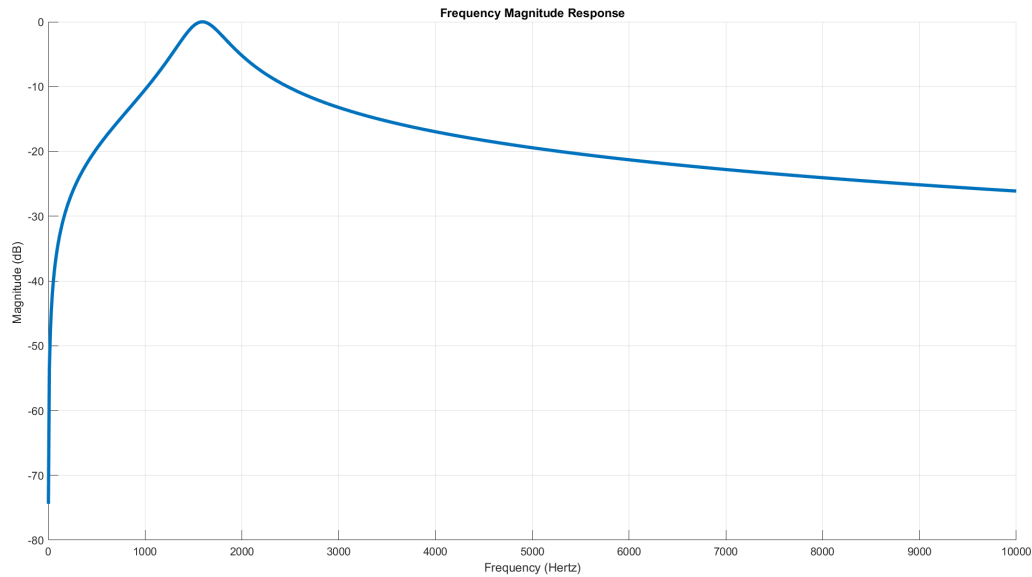


Figure 11: Frequency Response of a Band Pass Filter

6.3.2 ii.

As the resistor value set to 10K the plot given in Figure 12 is obtained.

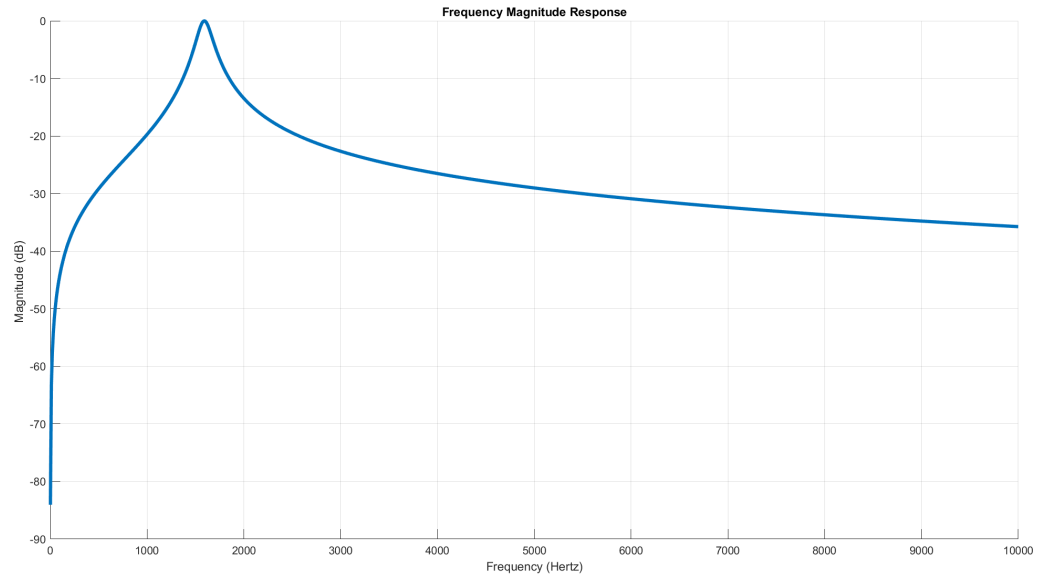


Figure 12: Frequency Response of a Band Pass Filter

6.3.3 iii.

Similarly for the square wave input with the response of our bandpass filter is obtained as given in Figure 13.

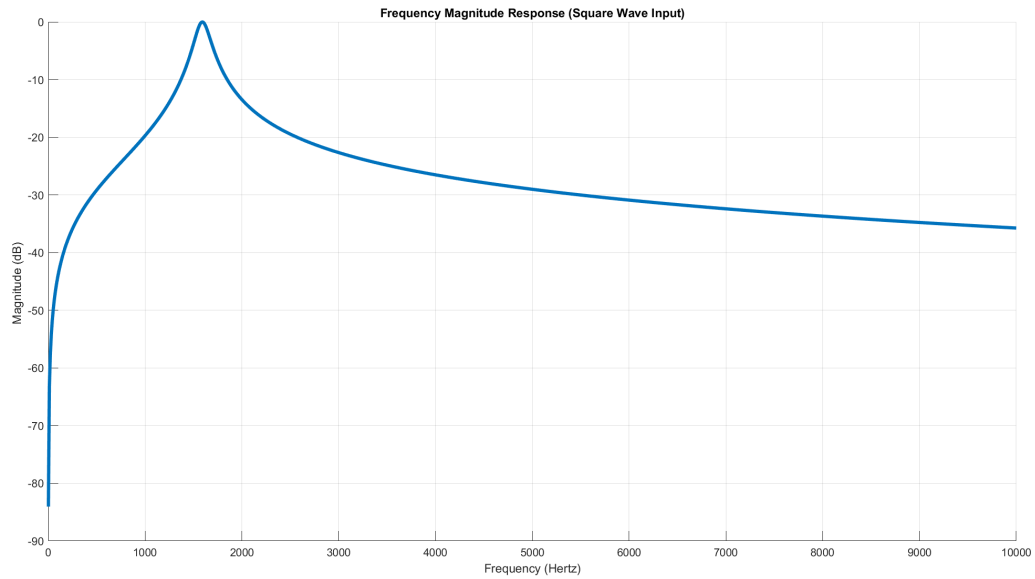


Figure 13: Frequency Response of a Band Pass Filter (square wave input)

7 Conclusion

In this preliminary document the characteristics of the filter topologies are investigated.

Appendix A

The results of the some of the simulations are fetched from LTSpice and plotted in MATLAB in order to make the plots more readable and convenient.