

Spring 2022 EE214 Experiment 1

Diodes and Rectifiers

Ahmet Akman 2442366
Yusuf Toprak Yıldiran 2444149

April 1, 2022

Contents

1 Introduction

In this experiment , characteristics of different diodes ,and rectifiers are investigated. First the i-v characteristics of 3 different diodes are expected to be oobserved. Then, the behavior of the half wave is expected to be experimented. Lastly, observations are made on clamper and zener regulator circuits. The results of the experimentation is presented in this document.

2 Experimental Results and Discussion

The results of the experiment are discussed in following steps.

2.1 Step 1

In this step, the circuit schematic given in Figure TODO is constructed on breadboard. As the signal supply, analog signal generator is used for floating output.

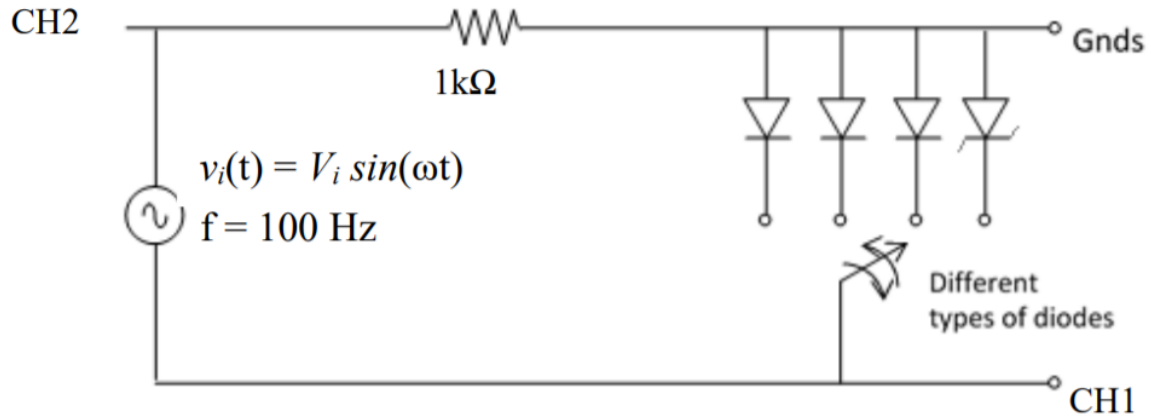


Figure 1: Circuit schematic for the step 1

2.1.1 a)

The diode models, [AA119](https://www.vishay.com/docs/88536/ba157.pdf), [BA159](https://www.vishay.com/docs/88536/ba157.pdf), and [BZX55C-6V2](https://www.vishay.com/docs/88536/ba157.pdf) are used. The probes of the oscilloscope is connected to the nodes indicated in Figure TODO. The resulting graph is plotted as given in Figure TODO2 TODO3, and TODO 4 for [AA119](https://www.vishay.com/docs/88536/ba157.pdf), [BA159](https://www.vishay.com/docs/88536/ba157.pdf), and [BZX55C-6V2](https://www.vishay.com/docs/88536/ba157.pdf) respectively.

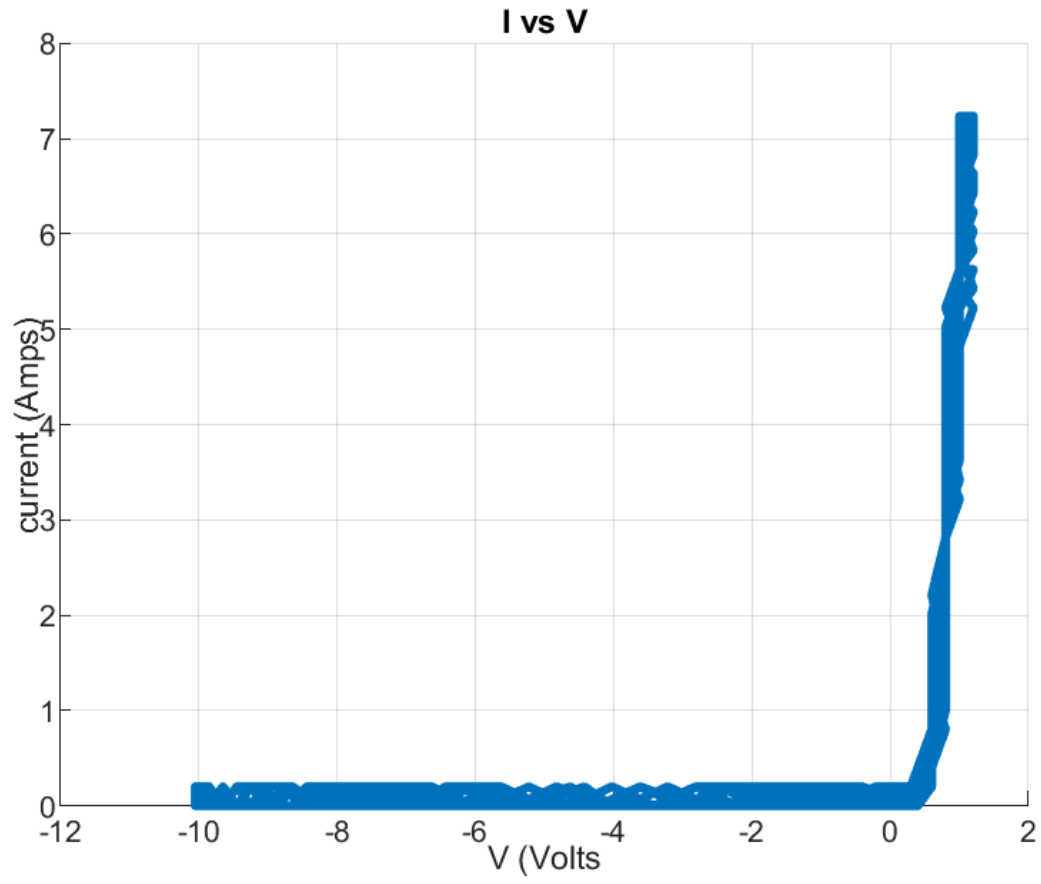


Figure 2: i-v characteristics of AA119

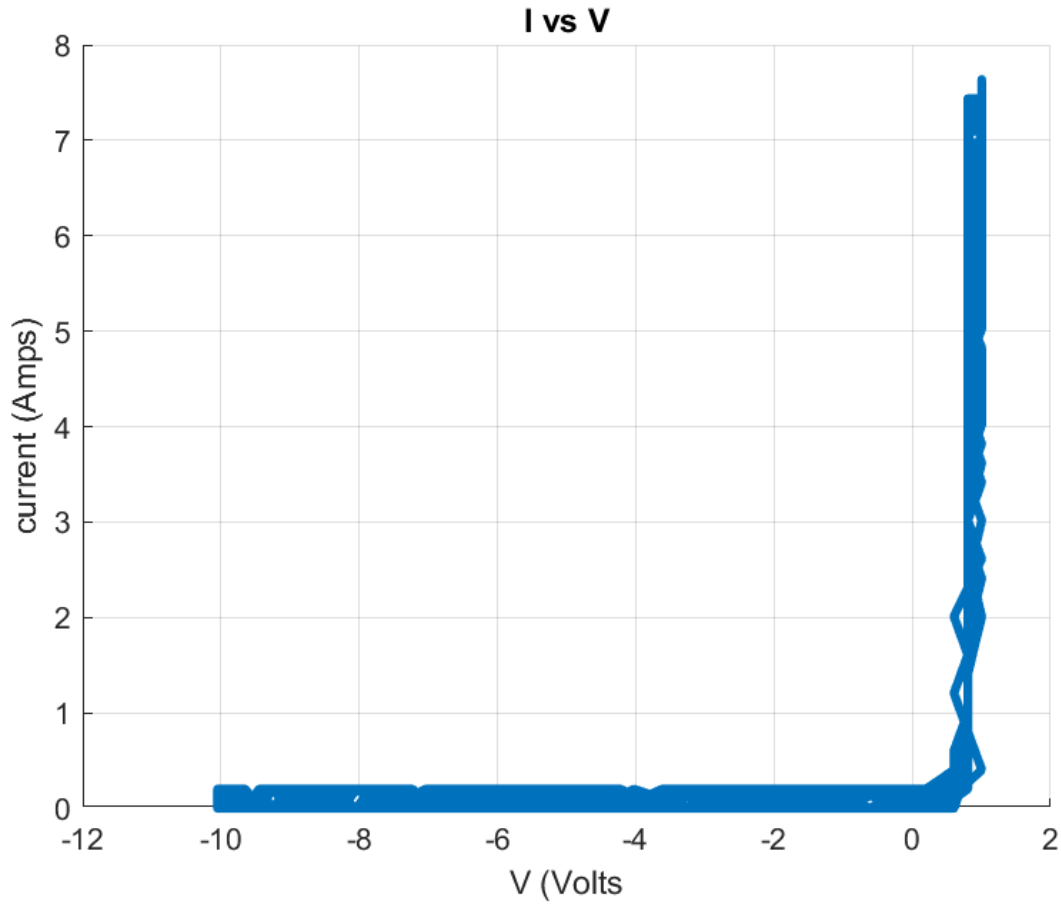


Figure 3: i-v characteristics of BA159

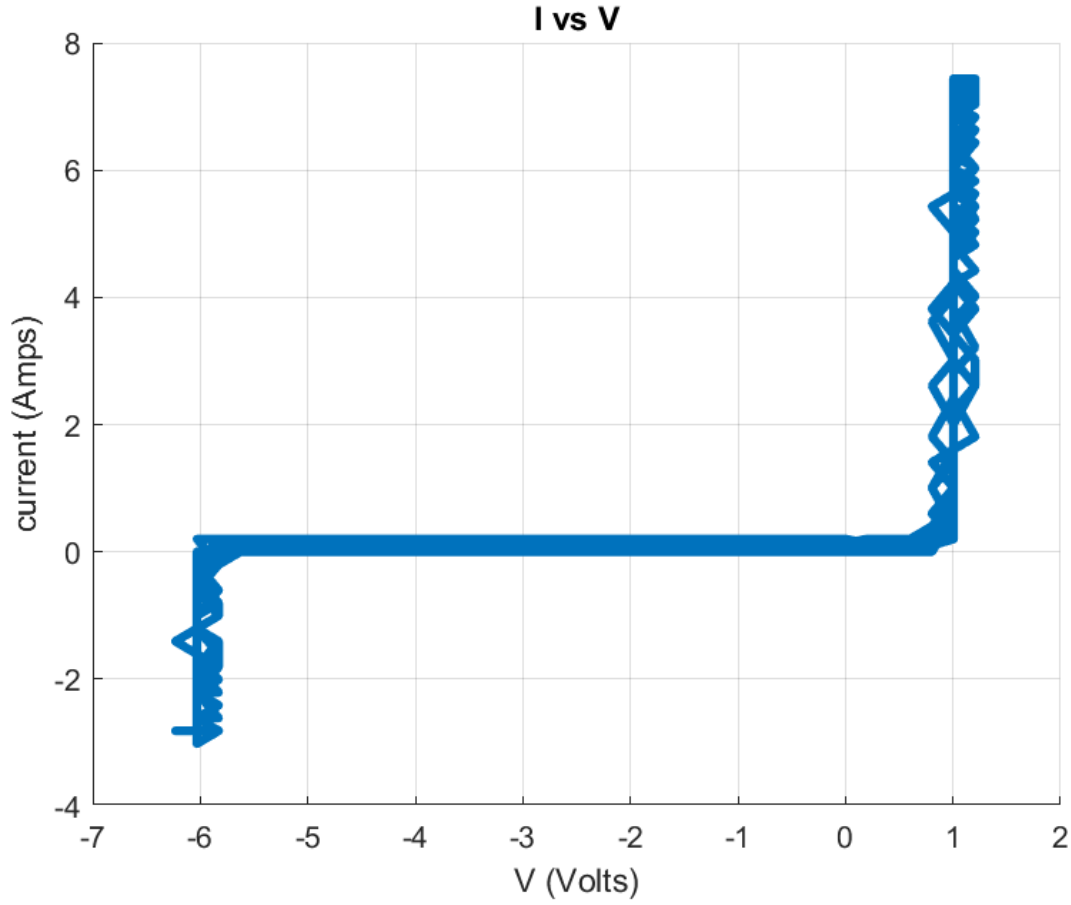


Figure 4: i-v characteristics of BZX55C-6V2

Using those plots the piecewise parameters of the diodes are obtained by the virtue of the cursors of the oscilloscope. The parameters of diode AA119 is given in Table 1.

Table 1: Piecewise parameters of diode AA119

V_{on}	350 mV
r_f	0.17 Ω
r_r	86 Ω

The obtained parameters of diode AA119 is given in Table 2.

Table 2: Piecewise parameters of diode BA159

V_{on}	973.5 mV
r_f	0.625 Ω
r_r	86.2 Ω

The obtained parameters of diode BZX55C-6V2 is given in Table 3.

Table 3: Piecewise parameters of diode BZX55C-6V2

V_{on}	752 mV
V_z	5.92V
r_f	0.05Ω
r_r	0.156Ω

So, the pimple i-v characteristics of 3 different diodes are obtained ,and analyzed using the plot.

2.1.2 b)

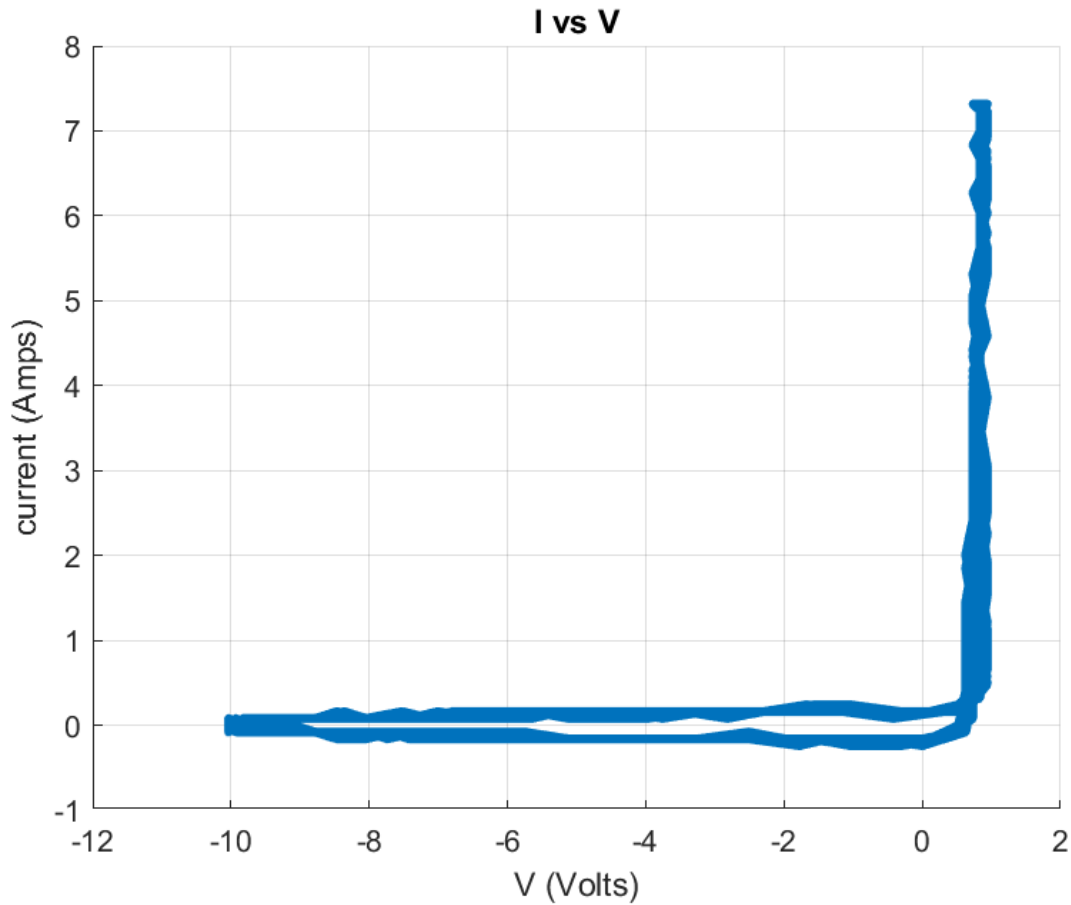


Figure 5: i-v characteristics of BA159 at 10khz

We can call separation of lines in i-v graph as hysteresis effect. When we increase frequency to 10kHz, we observed hysteresis effect on the i-v characteristics of diode on the DSO screen. Since our diode can not change its state as fast as our high frequency voltage source supply,

we observe this effect. To solve this problem and to be able to use diodes at high frequencies, there are "high speed" or "switching" diodes. These diodes can be used in high frequencies without observing hysteresis effect.

2.2 Step 2

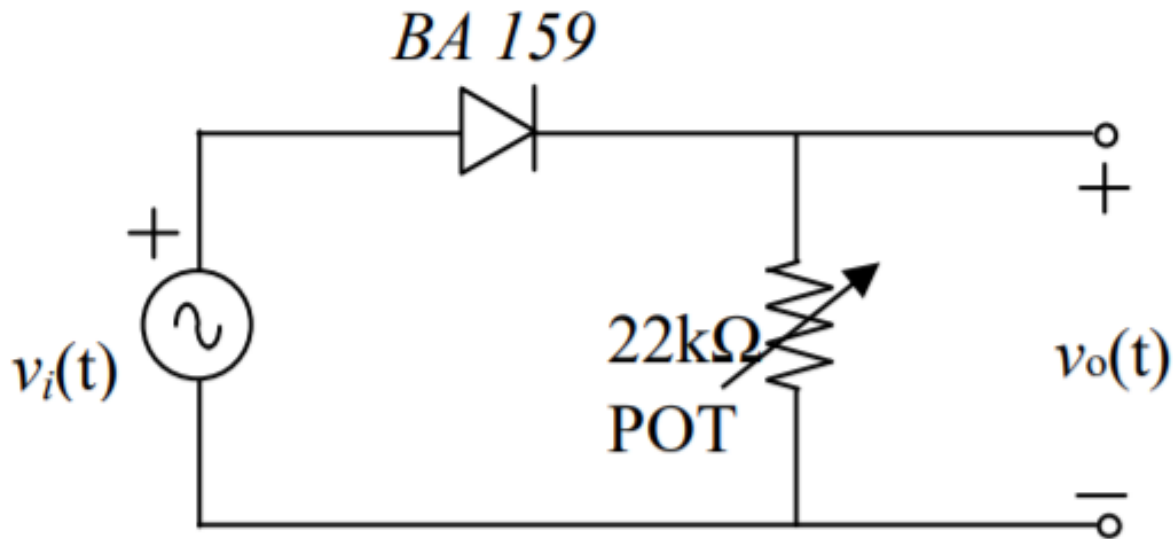


Figure 6: Circuit schematic for the step 2

For this part, we set the half-wave rectifier circuit given in Figure X and adjusted $v_i(t) = 2\sin(2000\pi t)V$

2.2.1 a)

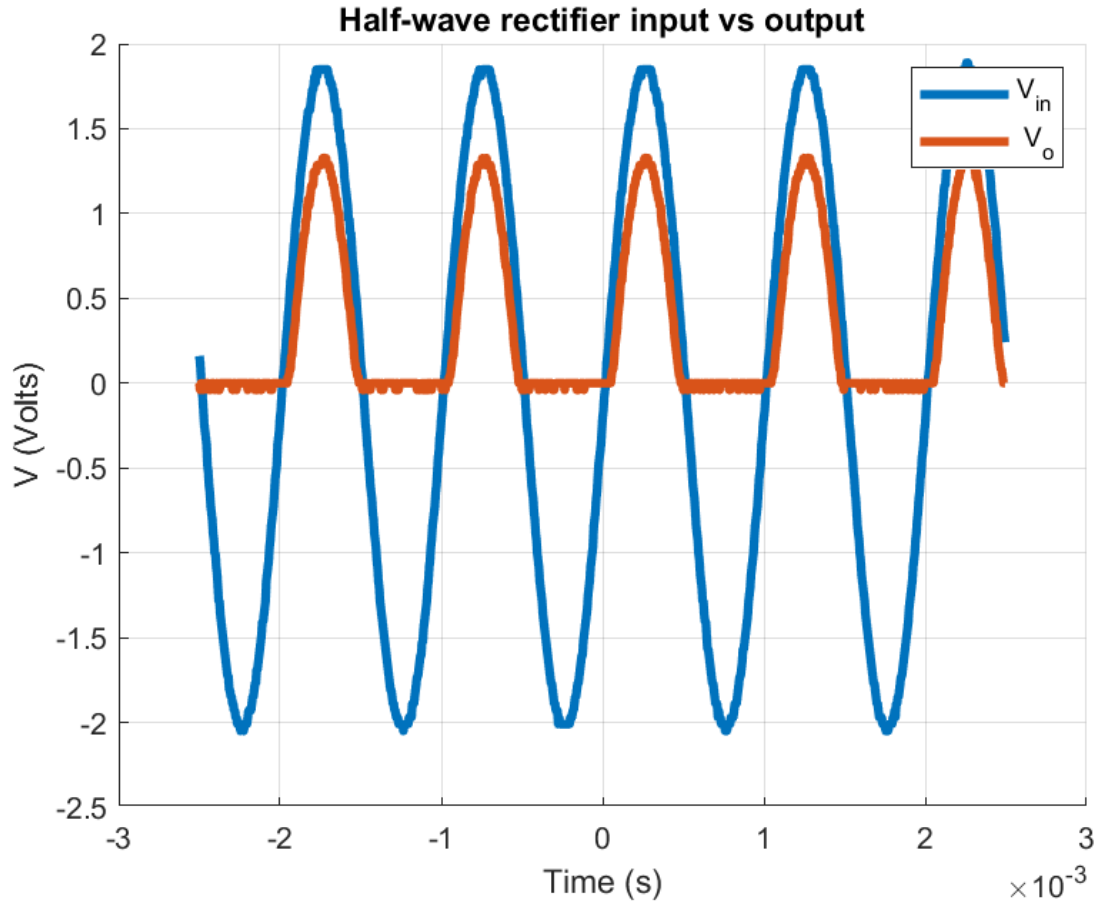


Figure 7: Half-wave rectifier with BA159

After setting POT to $1k\Omega$, we obtain output and input voltage waveforms on the graph indicated in Figure X.

If we look at the graph carefully, we can realize that output voltage is slightly lower than input voltage since the diode consumes energy. Then we measured the DC_{rms} of output value as 730mV using cursors of DSO. Output voltage waveform on the DSO screen is like the same with the input waveform in positive cycles but zero when input is in the negative cycle.

2.2.2 b)

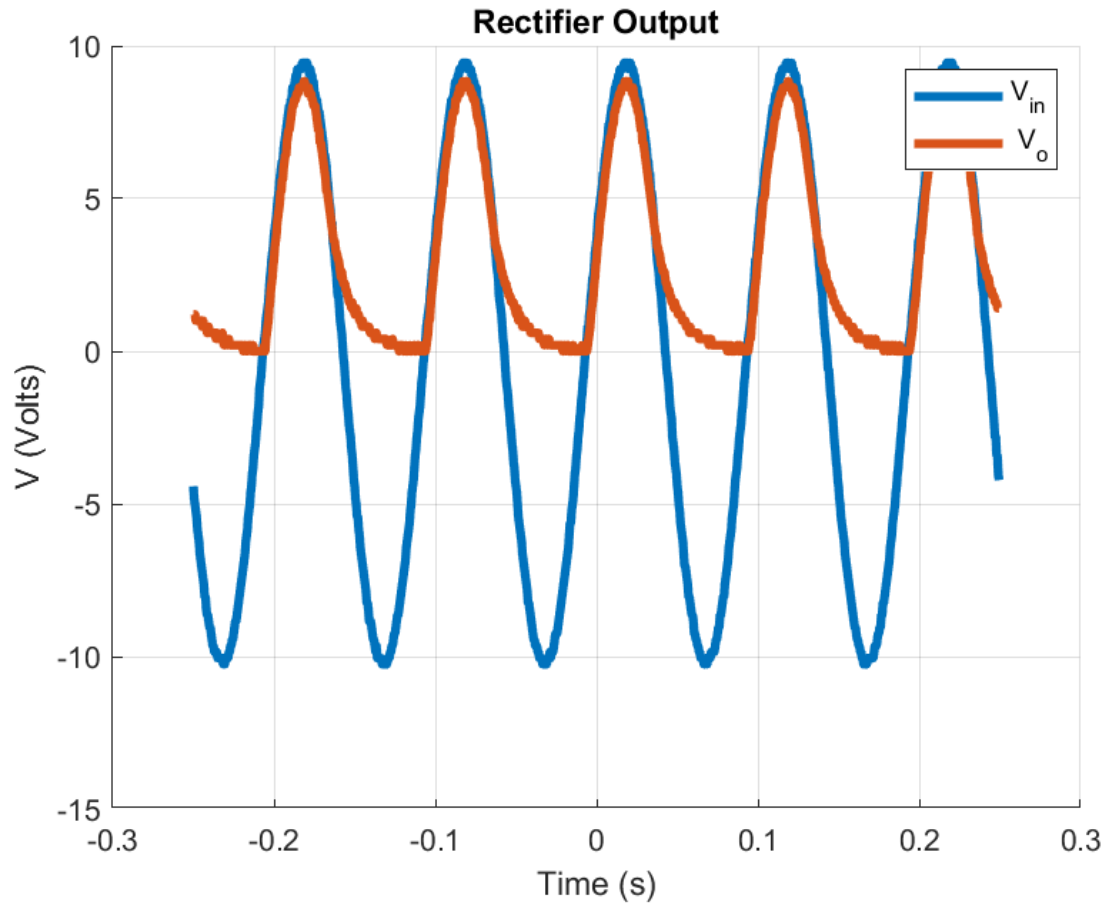


Figure 8: Half-wave rectifier with BA159 with pot set to 1.2K Ω

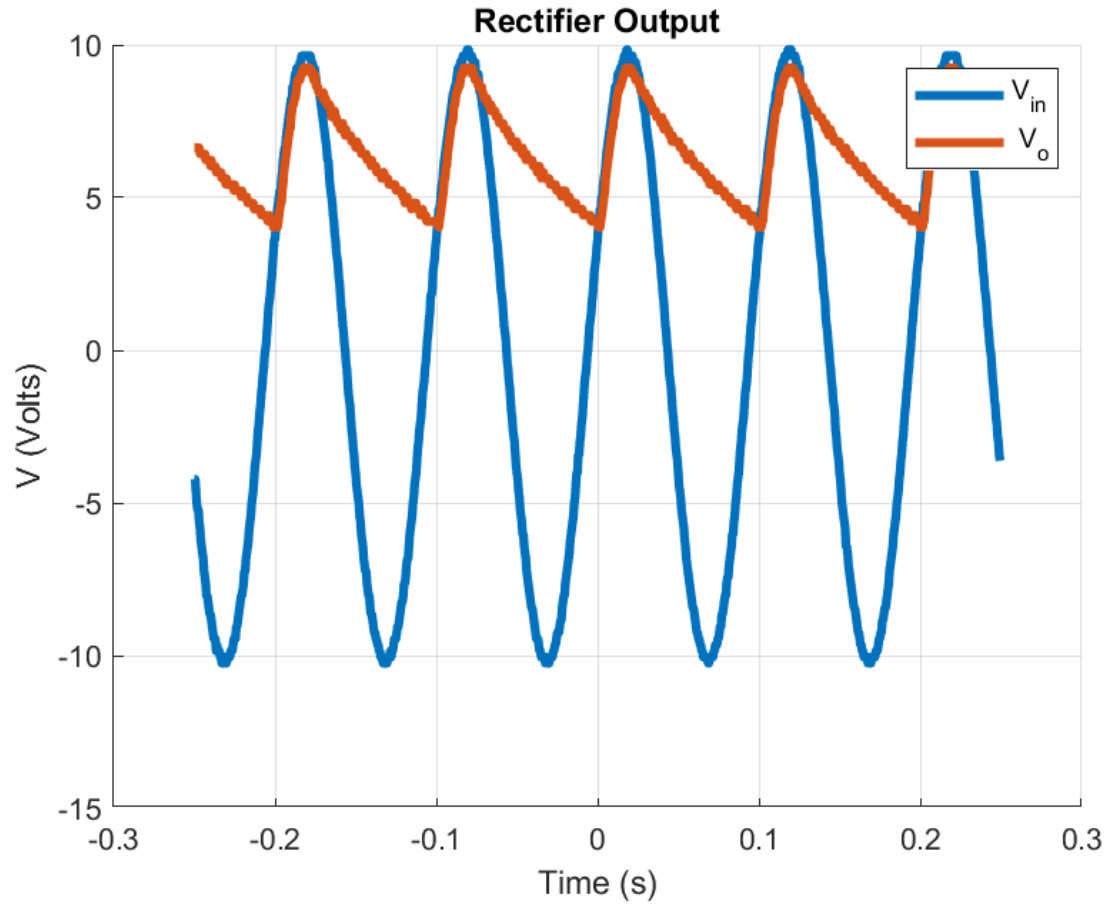


Figure 9: Half-wave rectifier with BA159 with pot set to 10K Ω

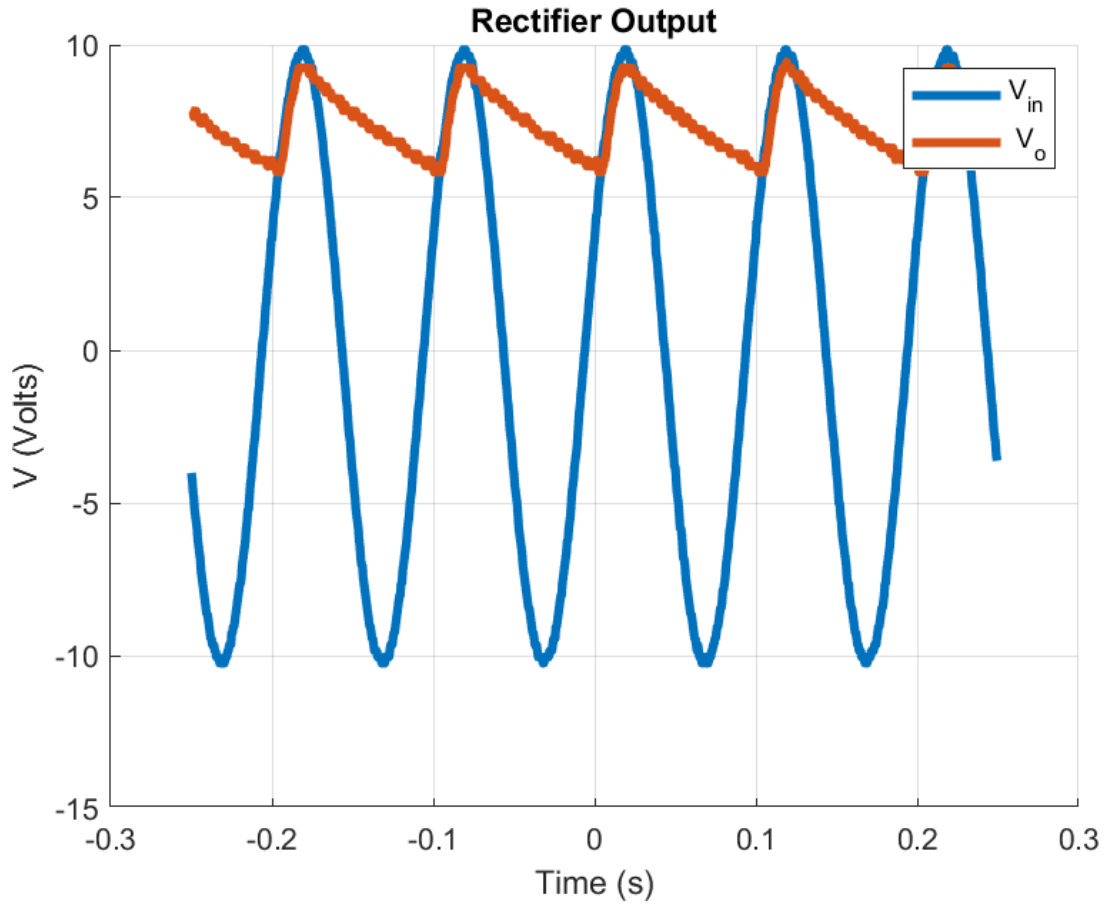


Figure 10: Half-wave rectifier with BA159 with pot set to 18K Ω

2.3 Step 3

In this third step, we set up the diode clamper circuit given in Figure X using the diode 1N4001 and set the voltage $v_i(t) = 10\sin(200\pi t)V$. Then plotted the input and output voltage waveforms on the graph given in Figure X.

From above graph we can derive that output waveform is just shifted form of input waveform to below zero. Since diode prevent capacitor from discharged, in order peak value of output to be clamped above zero diode should go into negative bias.

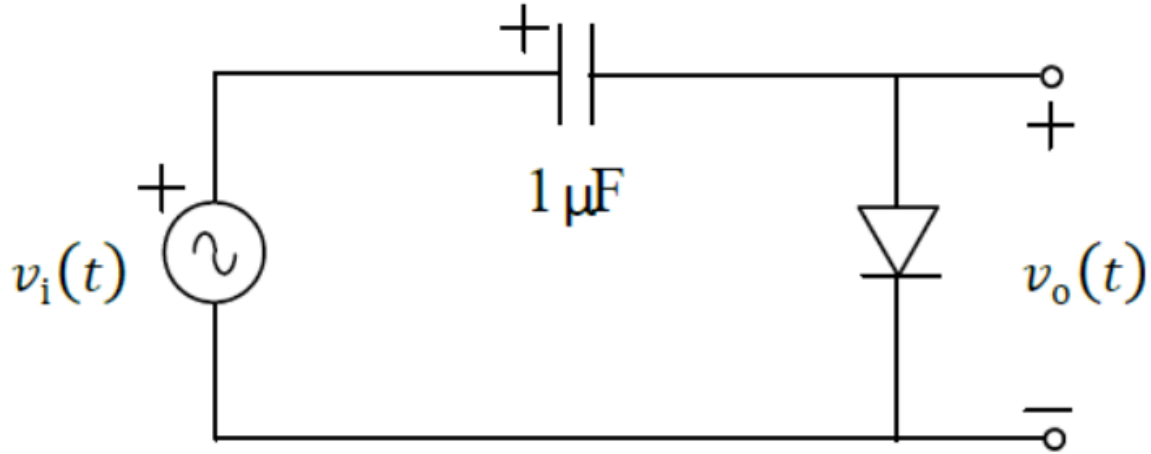


Figure 11: Circuit schematic for the step 3

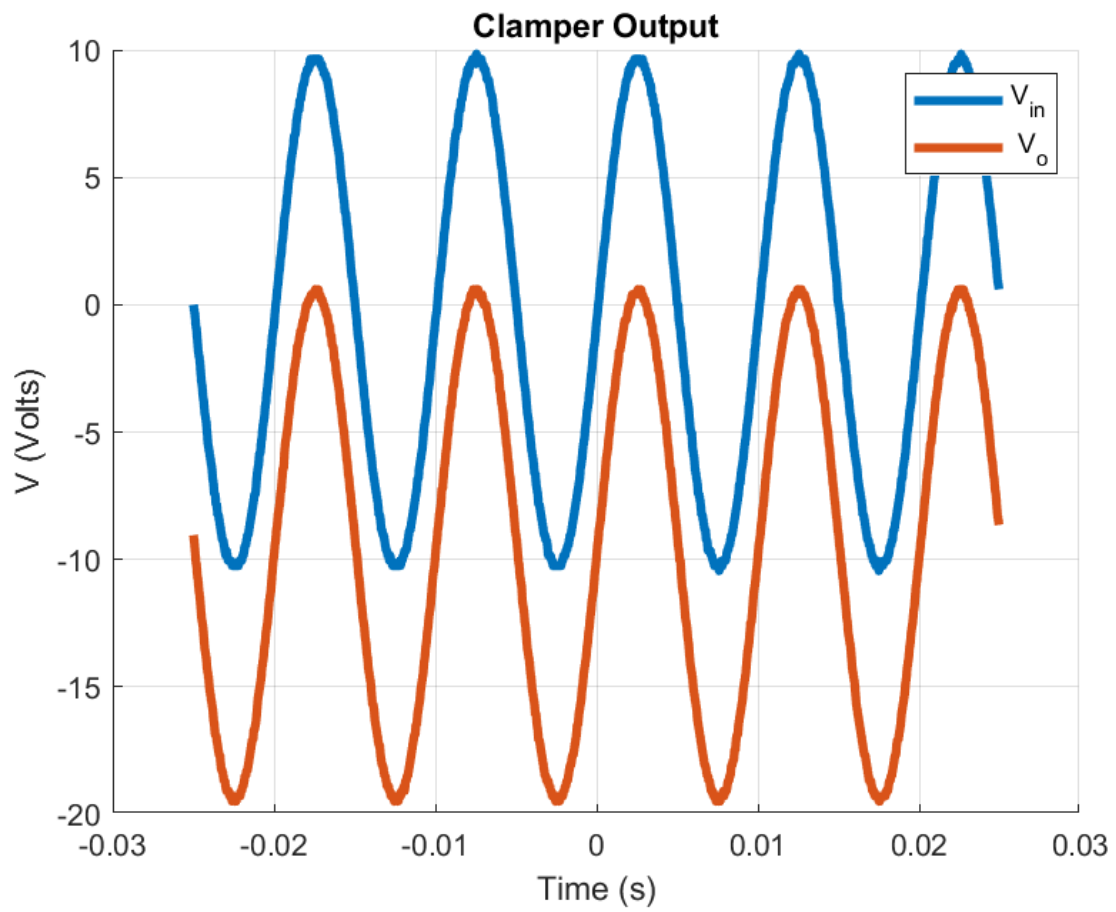


Figure 12: Clamper circuit output

2.4 Step 4

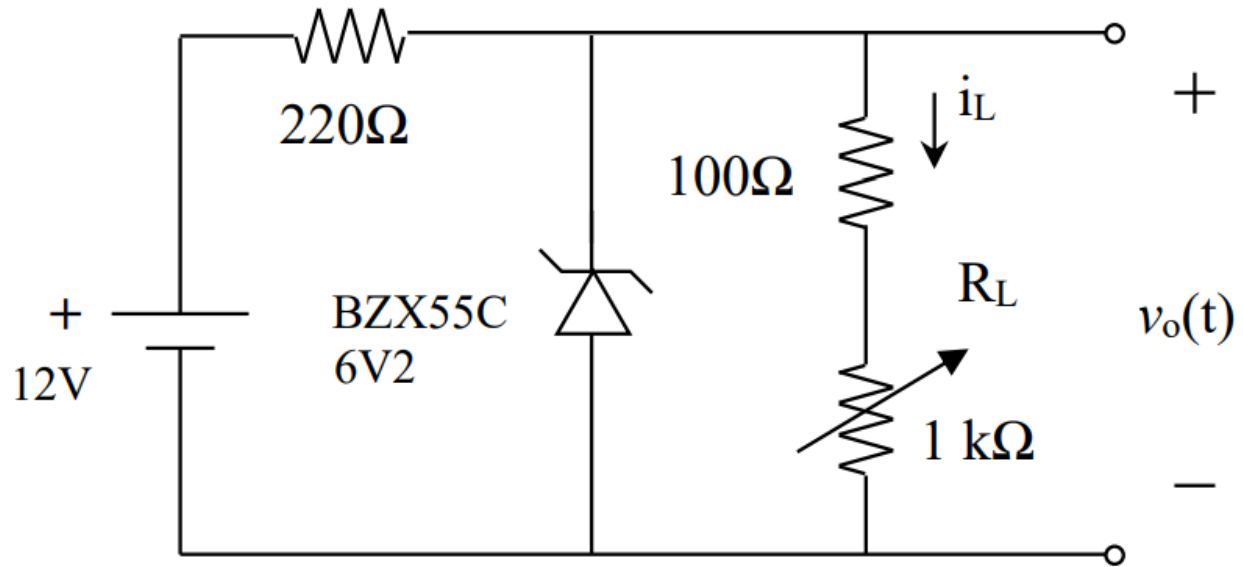


Figure 13: Circuit schematic for the step 4

3 Conclusion

asdfd

Appendix A

- PreLab Preparation 6 hours
- Experimental Work 2 hours
- Report Writing 6 hours