

Spring 2022 EE214 Experiment 4

Impedance Measurement and Complex Power

Ahmet Akman 2442366
Yusuf Toprak Yıldiran 2444149
Assistant: Onur Selim Kılıç

April 29, 2022

Contents

1	Introduction	1
2	Experimental Results and Discussion	1
2.1	Step 1	2
2.1.1	a.	2
2.1.2	b.	2
2.1.3	c.	2
2.1.4	d.	2
2.2	Step 2	3
2.3	Step 3	3
3	Conclusion	4

1 Introduction

2 Experimental Results and Discussion

The results of the experiment are discussed in the following steps.

2.1 Step 1

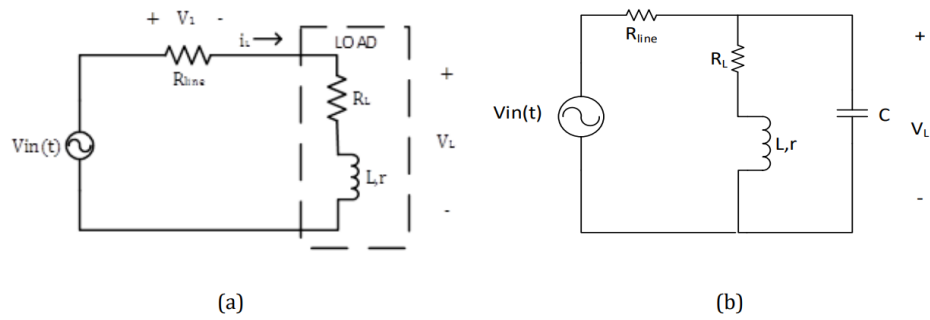


Figure 1: Circuit schematic for the step 1

2.1.1 a.

2.1.2 b.

2.1.3 c.

2.1.4 d.

Table 1: Power Measurements

Part	$V_{in}(\text{Vrms})$	$V_{line}(\text{Vrms})$	$V_{Load}(\text{Vrms})$	$i_{Load}(\text{mA rms})$	$\phi_{Load}(\text{degree})$	$\phi_{in}(\text{degree})$
a.						
b.						
c.						

Table 2: Power Calculations

Part	$P_{in}(\text{mW})$	$P_{line}(\text{mW})$	$P_{Load}(\text{mW})$	$Q_{Load}(\text{mVAR})$	$ S _{Load}(\text{mVA})$
a.					
b.					
c.					

Table 3: Load Parameters

Part a. (Load)			Part b. Load			Part c. Load		
pf	lead/lag	eff %	pf	lead/lag	eff %	pf	lead/lag	eff %

2.2 Step 2

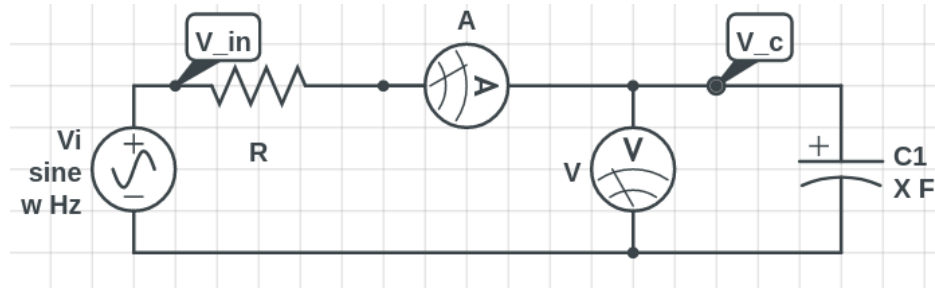


Figure 2: Circuit schematic for the step 2

2.3 Step 3

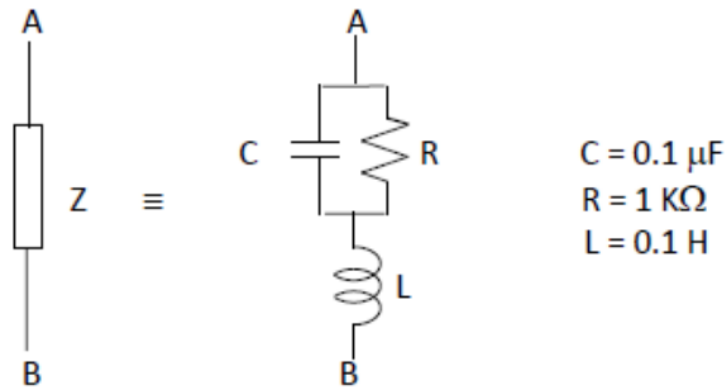


Figure 3: Circuit schematic for the step 3

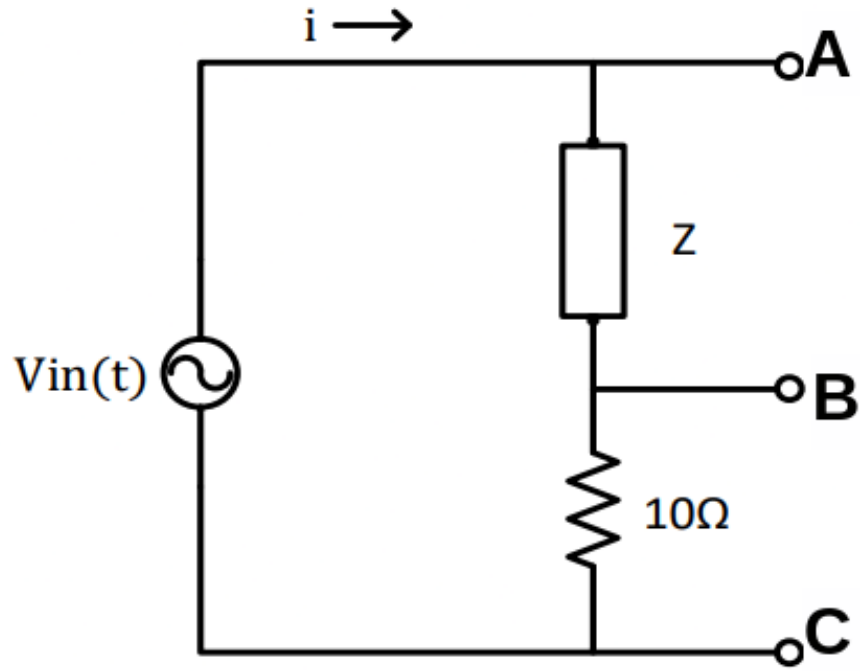


Figure 4: Outside circuit schematic for the step 3

3 Conclusion

Appendix A

- PreLab Preparation 3 hours
- Experimental Work 2 hours
- Report Writing 8 hours