

Spring 2022 EE214 Project Work

Preliminary Work

Ahmet Akman 2442366
Yusuf Toprak Yıldiran 2444149
Assistant: Onur Selim Kılıç

May 8, 2022

Contents

1	Introduction	1
2	Experimental Results and Discussion	1
2.1	Transmitter Unit	1
2.2	Receiver Unit	1
2.2.1	KHN Filter (State Variable Filter)	2
2.2.2	Sallen-Key Band Pass	2
2.2.3	Multiple Feedback Band Pass	2
2.3	Speaker Unit	2
3	Conclusion	2

1 Introduction

2 Experimental Results and Discussion

The results of the experiment are discussed in the following steps.

2.1 Transmitter Unit

2.2 Receiver Unit

In this part a receiver needed to be designed. So, let us first define the design requirements.

- The receiver should be able extract the desired signal amongst the signals with 12 different frequencies.

- The receiver should be able make a difference between the needed signal and others at least 10dB. (Closely related to the Q factor.)
- The receiver should provide option of channel adjustment with (at most) 2 potentiometer. Adjustment with 1 pot is the target.

In order to design a receiver unit that satisfies the fundamental requirements specified above, a circuit that only allows the signal with desired frequency to pass needed to be constructed. So , a filter design is expected which act like as a fourier transformer. There are passive and active filter designs which allows to pass below (low pass) or above (high pass) threshold frequencies. By combining those two filters one can build a filter which allows only certain band of signals. This is called band pass filter. Passive filters are not considered here since they would not be feasible in an adjustable setup. Now let us examine the active filters available in the literature to choose an optimum design path.

2.2.1 KHN Filter (State Variable Filter)

2.2.2 Sallen-Key Band Pass

2.2.3 Multiple Feedback Band Pass

2.3 Speaker Unit

3 Conclusion

Appendix A