

# Spring 2022 EE214 Project Work

## Preliminary Work

Ahmet Akman 2442366  
Yusuf Toprak Yıldiran 2444149  
Assistant: Onur Selim Kılıç

May 8, 2022

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Experimental Results and Discussion</b>	<b>1</b>
2.1	Transmitter Unit . . . . .	1
2.2	Receiver Unit . . . . .	1
2.2.1	Butterworth . . . . .	2
2.2.2	Chebyshev . . . . .	3
2.2.3	Bessel . . . . .	3
2.2.4	KHN Filter ( State Variable Filter) . . . . .	3
2.2.5	Sallen-Key Band Pass . . . . .	3
2.2.6	Multiple Feedback Band Pass . . . . .	3
2.3	Speaker Unit . . . . .	3
<b>3</b>	<b>Conclusion</b>	<b>3</b>

## 1 Introduction

## 2 Experimental Results and Discussion

The results of the experiment are discussed in the following steps.

### 2.1 Transmitter Unit

### 2.2 Receiver Unit

In this part a receiver needed to be designed. So, let us first define the design requirements.

- The receiver should be able extract the desired signal amongst the signals with 12 different frequencies.
- The receiver should be able make a difference between the needed signal and others at least 10dB. (Closely related to the Q factor.)
- The receiver should provide option of channel adjustment with (at most) 2 potentiometer. Adjustment with 1 pot is the target.

In order to design a receiver unit that satisfies the fundamental requirements specified above, a circuit that only allows the signal with desired frequency to pass needed to be constructed. So , a filter design is expected which act like as a fourier transformer. There are passive and active filter designs which allows to pass below (low pass) or above (high pass) threshold frequencies. By combining those two filters one can build a filter which allows only certain band of signals. This is called band pass filter.

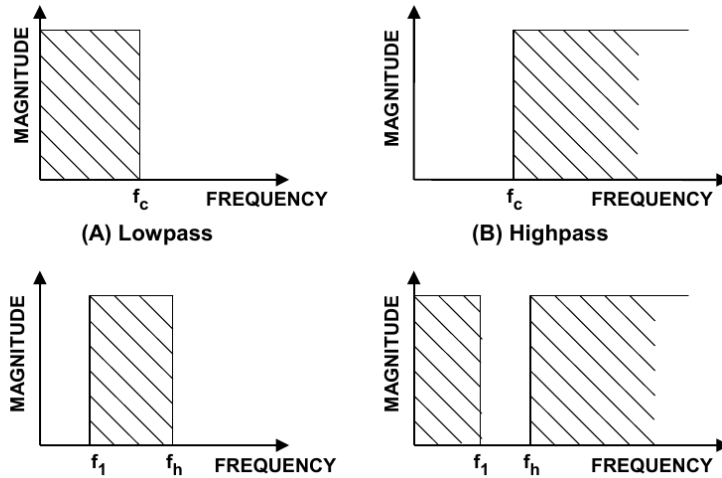


Figure 1: Filter Responses (ideal)

Passive filters are not considered here since they would not be feasible in an adjustable setup. The transfer function of band-pass filter can be explained as following.

$$H(s) = \frac{H_0(\omega_0)^2}{s^2 + \frac{\omega_0}{Q}s + (\omega_0)^2}$$

Now let us examine briefly transfer responses in the literature to choose an optimum design path.

### 2.2.1 Butterworth

Butterworth transfer response offers clean pass and not-pass regions in other words no ripple. However, the band that allows the signals is not narrow.

### **2.2.2 Chebyshev**

Chebyshev transfer response offers narrower band however it has ripples in the pass band.

### **2.2.3 Bessel**

Bessel filter is optimized to obtain better transient response due to a linear phase (i.e. constant delay) in the passband.

For our case as long as it is tuned carefully all three transfer responses can be used. However in order to have better frequency discrimination Chebyshev function is selected to be used in this phase of the project. The values for the Chebyshev function will be fetched from the design tables available in internet. (The table is not included here in order not to excess page limit.)

Now let us examine briefly the available design topologies to choose which design path to go for.

### **2.2.4 KHN Filter ( State Variable Filter)**

### **2.2.5 Sallen-Key Band Pass**

### **2.2.6 Multiple Feedback Band Pass**

## **2.3 Speaker Unit**

# **3 Conclusion**

# **Appendix A**