

Spring 2022 EE214 Experiment 1

Diodes and Rectifiers

Ahmet Akman 2442366
Yusuf Toprak Yıldiran 2444149

March 30, 2022

Contents

1	Introduction	1
2	Experimental Results and Discussion	1
2.1	Step 1	2
2.1.1	a)	2
2.1.2	b)	3
2.2	Step 2	3
2.2.1	a)	4
2.2.2	b)	4
2.3	Step 3	4
2.4	Step 4	4
3	Conclusion	5

1 Introduction

In this experiment , characteristics of different diodes ,and rectifiers are investigated. First the i-v characteristics of 3 different diodes are expected to be oobserved. Then, the behavior of the half wave is expected to be experimented. Lastly, observations are made on clamper and zener regulator circuits. The results of the experimentation is presented in this document.

2 Experimental Results and Discussion

The results of the experiment are discussed in following steps.

2.1 Step 1

In this step, the circuit schematic given in Figure TODO is constructed on breadboard. As the signal supply, analog signal generator is used for floating output.

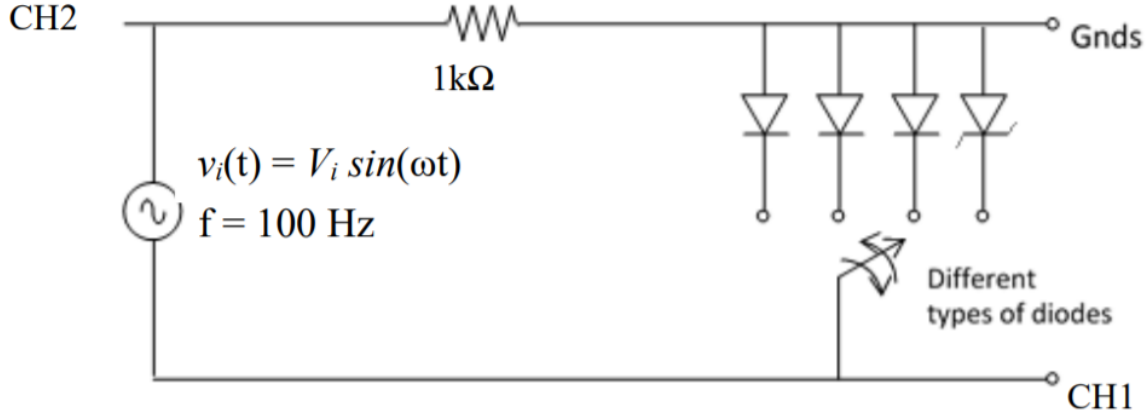


Figure 1: Circuit schematic for the step 1

2.1.1 a)

The diode models, [AA119](https://www.vishay.com/docs/88536/ba157.pdf), [BA159](https://www.vishay.com/docs/88536/ba157.pdf), and [BZX55C-6V2](https://www.vishay.com/docs/88536/ba157.pdf) are used. The probes of the oscilloscope is connected to the nodes indicated in Figure TODO. The resulting graph is plotted as given in Figure TODO2 TODO3, and TODO 4 for [AA119](https://www.vishay.com/docs/88536/ba157.pdf), [BA159](https://www.vishay.com/docs/88536/ba157.pdf), and [BZX55C-6V2](https://www.vishay.com/docs/88536/ba157.pdf) respectively. Using those plots the piecewise parameters of the diodes are obtained by the virtue of the cursors of the oscilloscope. The parameters of diode AA119 is given in Table 1.

Table 1: Piecewise parameters of diode AA119

V_{on}	350 mV
r_f	0.17 Ω
r_r	86 Ω

The obtained parameters of diode AA119 is given in Table 2.

Table 2: Piecewise parameters of diode BA159

V_{on}	973.5 mV
r_f	0.625 Ω
r_r	86.2 Ω

The obtained parameters of diode BZX55C-6V2 is given in Table 3.

Table 3: Piecewise parameters of diode BZX55C-6V2

V_{on}	752 mV
V_z	5.92V
r_f	0.05 Ω
r_r	0.156 Ω

So, the pimple i-v characteristics of 3 different diodes are obtained ,and analyzed using the plot.

2.1.2 b)

2.2 Step 2

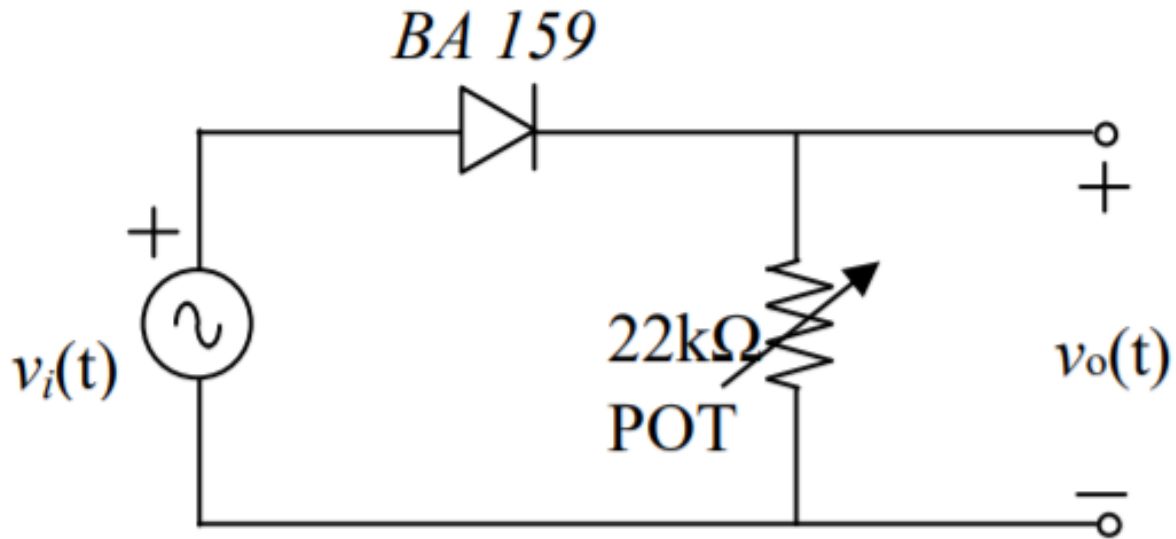


Figure 2: Circuit schematic for the step 2

2.2.1 a)

2.2.2 b)

2.3 Step 3

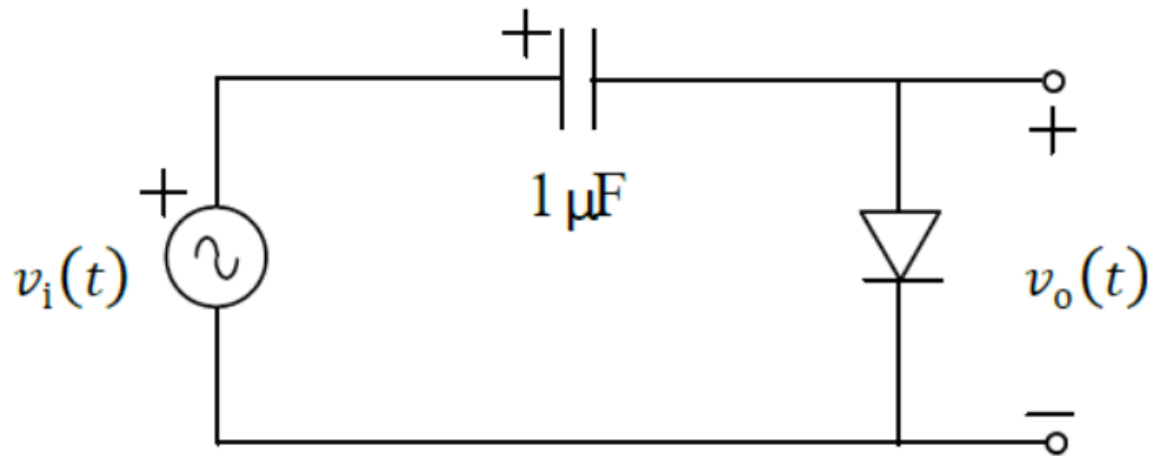


Figure 3: Circuit schematic for the step 3

2.4 Step 4

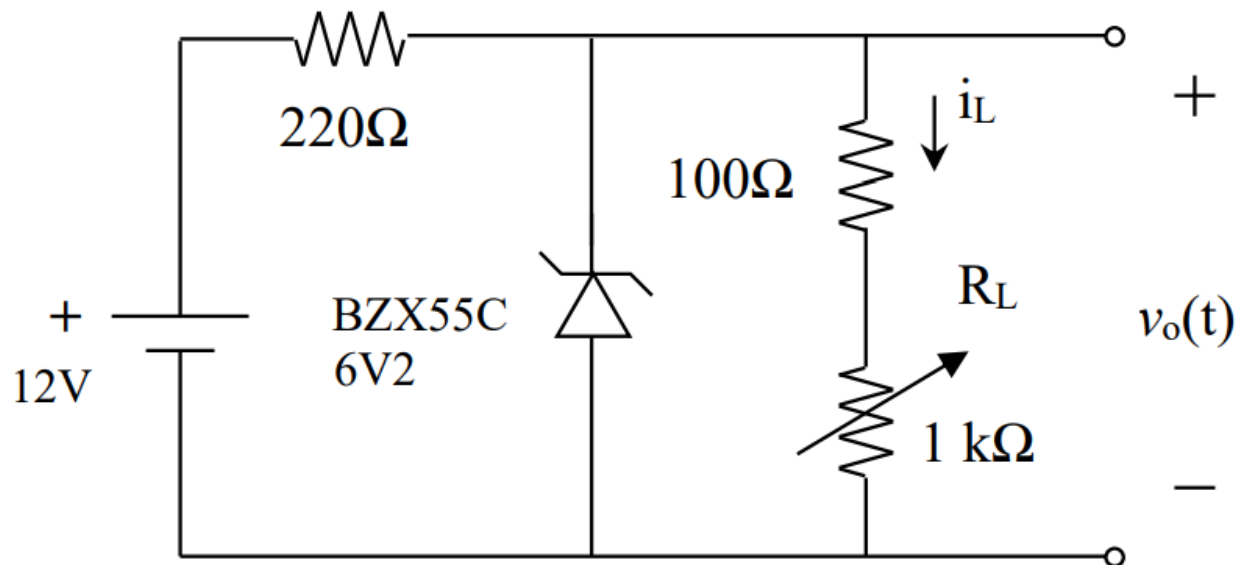


Figure 4: Circuit schematic for the step 4

3 Conclusion

asdfd

Appendix A

- PreLab Preprataion 6 hours
- Experimental Work 2 hours
- Report Wrining 6 hours