

Spring 2022 EE214 Experiment 1

Diodes and Rectifiers

Ahmet Akman 2442366
Yusuf Toprak Yıldiran 2444149

March 30, 2022

Contents

1 Introduction

In this document the actions corresponding requirements defined in the Experiment Manual are represented.

2 Experimental Results and Discussion

2.1 Step 1

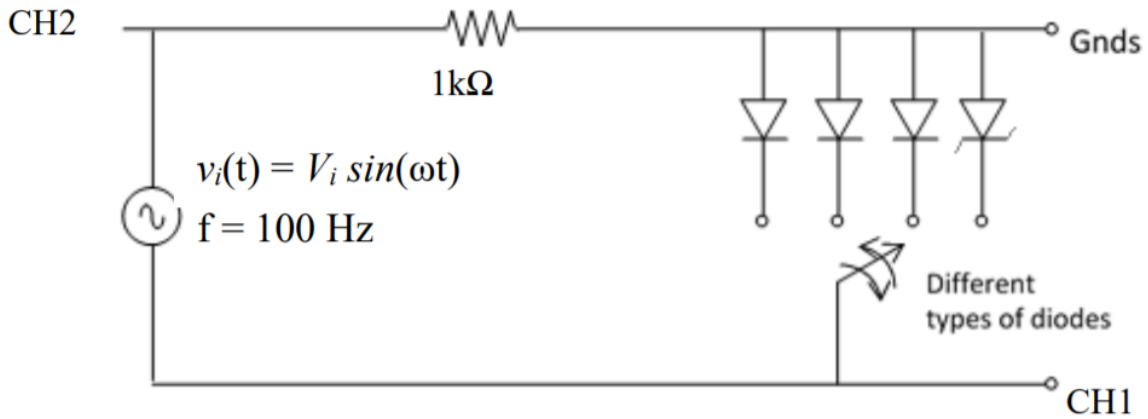


Figure 1: Circuit schematic for the step 1

2.1.1 a)

2.1.2 b)

2.2 Step 2

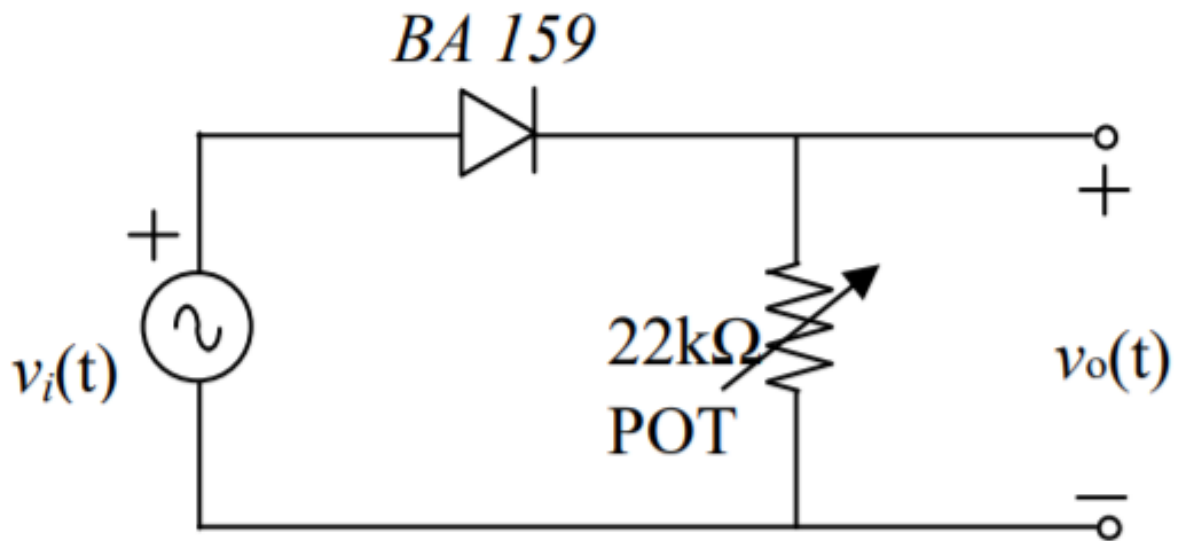


Figure 2: Circuit schematic for the step 2

2.2.1 a)

2.2.2 b)

2.3 Step 3

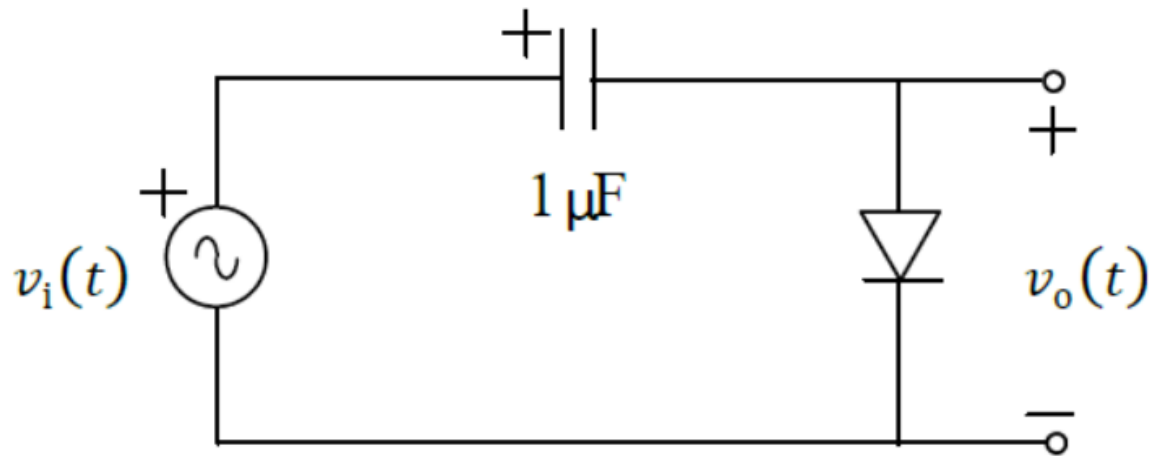


Figure 3: Circuit schematic for the step 3

2.4 Step 4

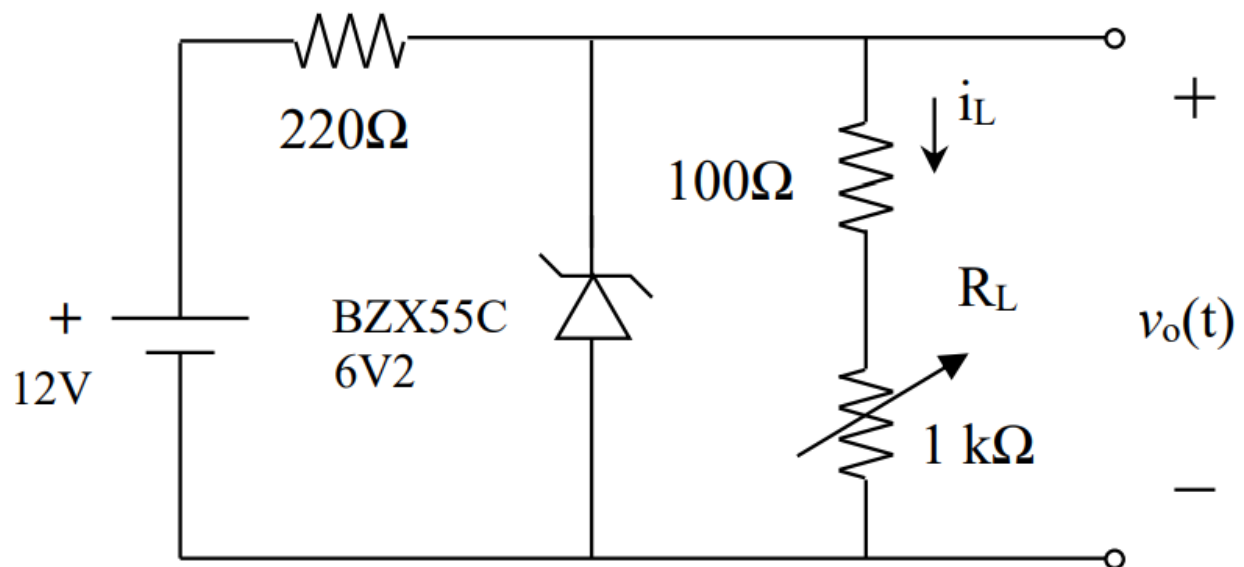


Figure 4: Circuit schematic for the step 4

3 Conclusion

asdfd

Appendix A

- PreLab Preprataion 6 hours
- Experimental Work 2 hours
- Report Wrining 6 hours